 


Class	:	
Batch	:	
Roll. No	:	
ABC ID	:	
Assignment No.	:	B.3.a
Assignment Name	:	CMOS TRANSMISSION-GATE (TG)
Date Of Performance	:	

Block Diagram:-




C = Control Signal (Applied to Gate of NMOS)

\overline{C} = Inverted Control Signal (Applied to Gate of PMOS)

$C = 1$: NMOS = PMOS = ON

O/P Node is Connected to I/P Node


MOSFET-LEVEL SCHEMATIC of TG:-

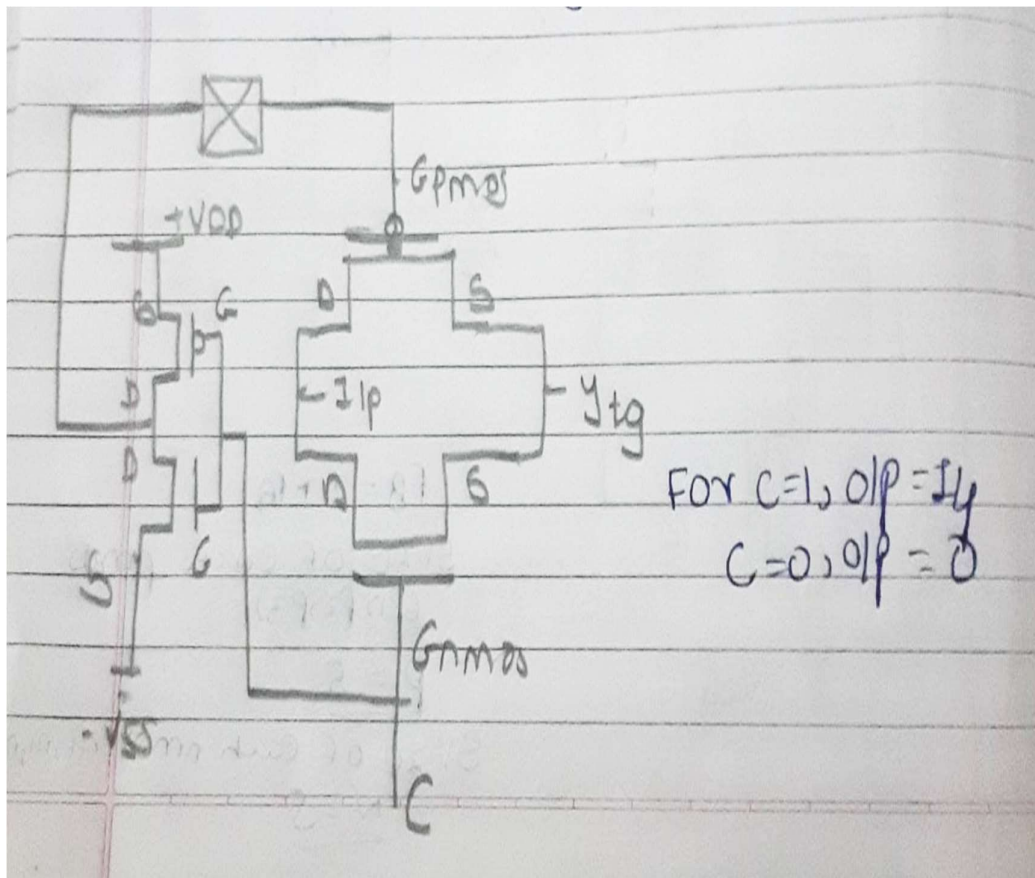

Truth Table:-


C	Y_{tg}
1	I/P
0	NO CHANGE

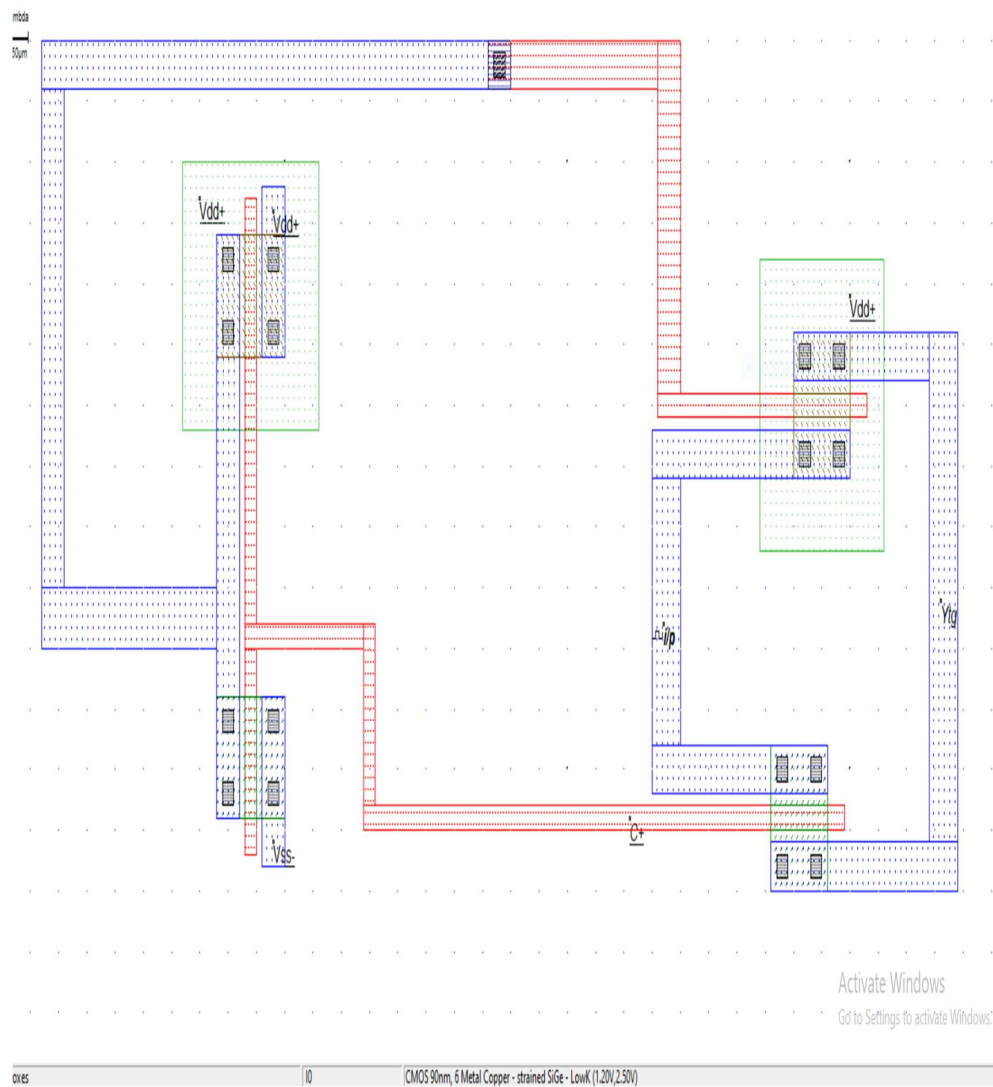Layout (90 nm Foundry) : ($V_{dd} = 1.2\text{ V}$)



Waveform:


1) For C=1

 

O/P = S-1 (For I/P = 1)

O/P = S-0 (For I/P = 0)

2) For C=0

 

O/P Shows NO CHANGE in spite of Changes in I/P ,as O/P Node is DISCONNECTED from I/P Node

Conclusion:-

- 1) Drawn the LAYOUT for CMOS TRANSMISSION GATE (TG) using 90 nm Foundry.
- 2) Being a **Pure-CMOS System** (PMOS // NMOS & CMOS INVERTER) , it gives both **S-1 & S-0** as O/P.
- 3) **Power Dissipation** in Enabled Condition (C = 1) is just **0.019 μ W** thus exhibiting the Merit of Very Low Power Dissipation of CMOS Logic Family.
- 4) Power Dissipation in Disabled Condition (C = 0) is Very High (**1.494 μ W**)
- 5) Simulated the LAYOUT to observe waveforms & verified its functionality as per TRUTH-TABLE.