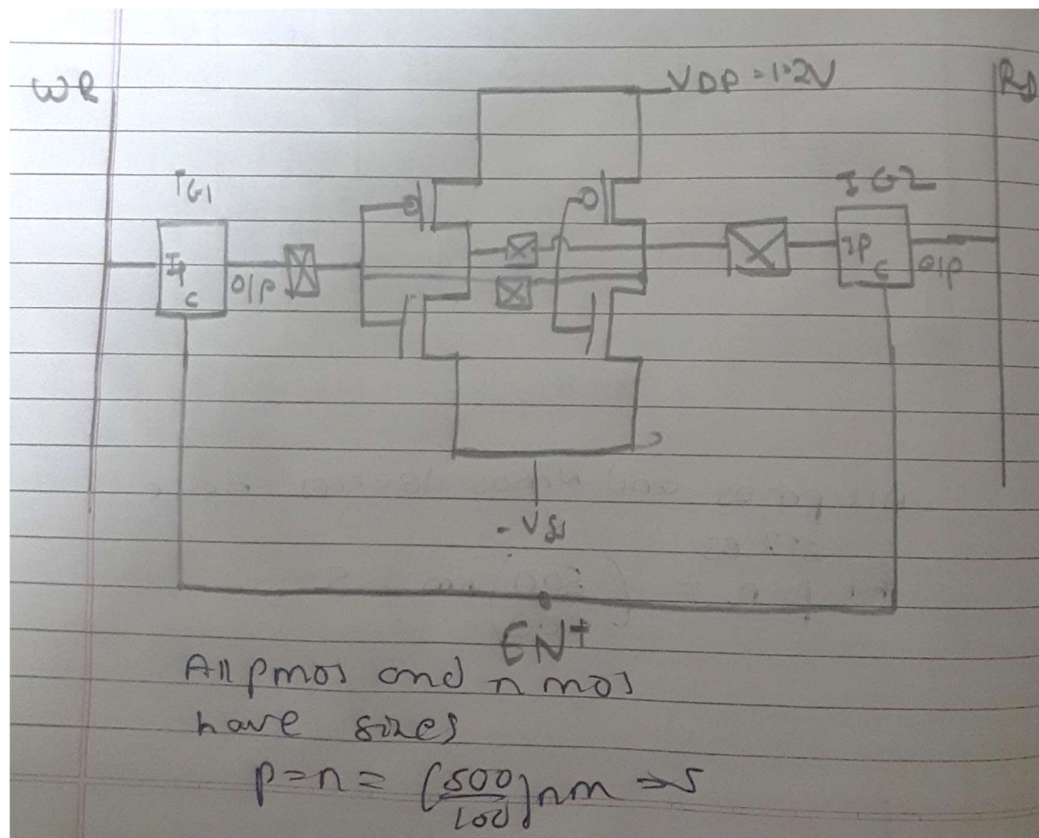


Class	:	
Batch	:	
Roll. No	:	
ABC ID	:	
Assignment No.	:	B.4.b
Assignment Name	:	1-bit SRAM (Using TG S/W)
Date Of Performance	:	

MOSFET-LEVEL SCHEMATIC of 1-bit SRAM Cell Using TG S/W :-




In the above Schematic :

- ✚ TG1 , TG2 : TG S/W's
- ✚ I1 , I2 : CROSS – COUPLED CMOS INVERTERS
- ✚ System is a PURE CMOS SYSTEM
- ✚ WR-line gets connected to RD line through TG1 , TG2 & I1-I2 pair
- ✚ TG1 = TG2 = ON / OFF , for C = EN = 1 / 0
- ✚ TG1 , TG2 Transmit "1" as STRONG-1 & "0" as STRONG-0
- ✚ I1 , I2 Transmit "1" as STRONG-0 , "0" as STRONG-1

Truth Table:-


EN	WR	RD
1	0	STRONG-1
1	1	STRONG-0
0	X	HOLD

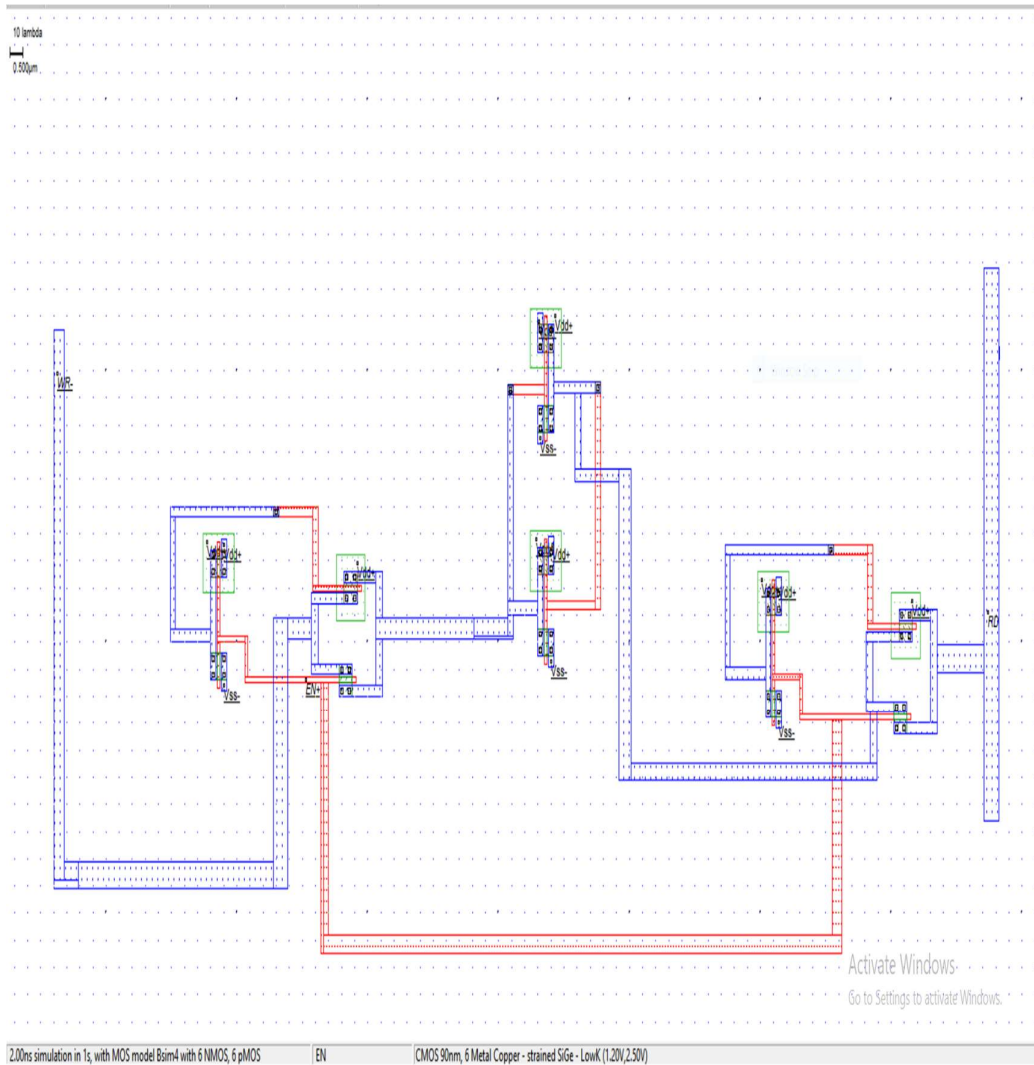Layout (90 nm Foundry) : ($V_{dd} = 1.2\text{ V}$)




Waveform:

 1) $EN=1, WR = 0, RD = \text{STRONG-1}$ ($RD = V_{dd} = 1.2 \text{ V}$)



 2) $EN=1, WR = 1, RD = \text{STRONG-0}$ ($RD = -V_{ss} = 0 \text{ V}$)



3) EN=0, WR = 0 / 1 , RD = **HOLD (NO CHANGE)**



Conclusion :-

- 1) Drawn the LAYOUT of 1-bit SRAM Cell Using TG S/W's for 90 nm Foundry.
- 2) Being a **Pure-CMOS System** (TG S/W's & CMOS INVERTERS) , it gives **RD = S-1 / S-0** for **WR = 0 / 1** respectively.
- 3) So , **"0"** is **READ** as **S-1** (*Acceptable*) & **"1"** is **READ** as **S-0** (*Acceptable*)
- 4) **The reason for above is the Presence of TG S/W's on both sides of CMOS INVERTERS (A Pure CMOS System)**